Lecture 7: Circuit Graphs, the Incidence Matrix and Tellegen's Theorem

EE201 – Circuit Theory I

M. Mert Ankaralı

Department of Electrical and Electronics Engineering
Middle East Technical University

current voltage power nodes

Interconnection equations

A circuit with b branches: $2b$ unknowns, v_k and i_k for each branch k.

Group	How many	Describes
element equations	b	*what* each element is: $v = Ri$, a source value, ...
interconnection equations	b	*how* they are wired: $n-1$ KCL, $b-n+1$ KVL

Interconnection equations

A circuit with b branches: $2b$ unknowns, v_k and i_k for each branch k.

Group	How many	Describes
element equations	b	*what* each element is: $v = Ri$, a source value, ...
interconnection equations	b	*how* they are wired: $n-1$ KCL, $b-n+1$ KVL


KCL and KVL do not care what the elements are

Replace a resistor by a capacitor or a source, keep the wiring: KCL and KVL stay the same. Keep only the wiring — the graph — and write all KCL equations as one matrix equation.

The graph of a circuit

Each element is a branch, each meeting point a node.

Procedure

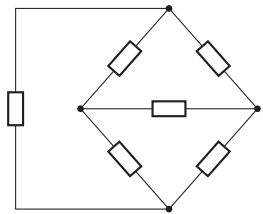

bridge circuit


Six elements, drawn as boxes: their type does not matter here.

The graph of a circuit

Each element is a branch, each meeting point a node.

Procedure

1. Label each branch: $1, \ldots, b$.

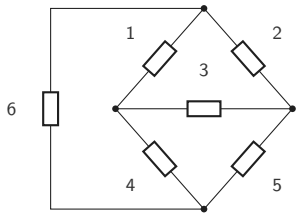

bridge circuit


Branches $1, \ldots, 6$: $b = 6$.

The graph of a circuit

Each element is a branch, each meeting point a node.

Procedure

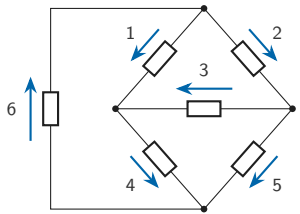1. Label each branch: $1, \ldots, b$.
2. Give each branch a direction — arbitrary.



bridge circuit


The arrow is the reference direction of i_k; v_k has $+$ at the tail.
If the current flows the other way, i_k is simply negative.

The graph of a circuit

Each element is a branch, each meeting point a node.

Procedure

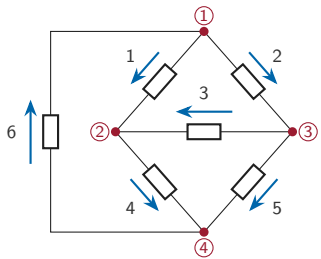1. Label each branch: $1, \ldots, b$.
2. Give each branch a direction — arbitrary.
3. Label each node: ①, …, ⓝ.



bridge circuit


Nodes ①, ②, ③, ④: $n = 4$.

The graph of a circuit

Each element is a branch, each meeting point a node.

Procedure

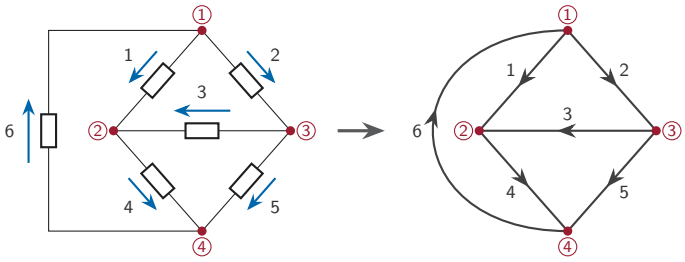1. Label each branch: $1, \ldots, b$.
2. Give each branch a direction — arbitrary.
3. Label each node: ①, …, ⓝ.
4. Draw the graph: dots and arrows.




Keep only dots and arrows: $n = 4$, $b = 6$.
Branch 6 is curved only for clarity — a straight arrow is the same graph.

Elements with more than two terminals

A k-terminal element

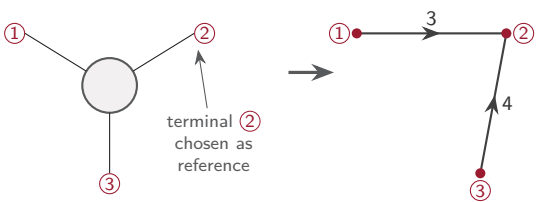
Choose one terminal as its reference (arbitrary). Draw $k-1$ branches, one from each other terminal to the reference terminal.



Elements with more than two terminals

A k-terminal element

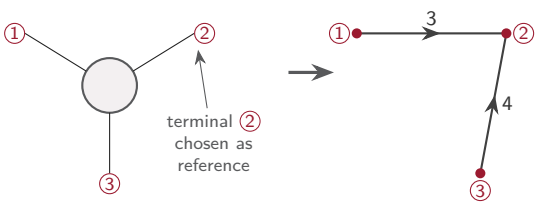Choose one terminal as its reference (arbitrary). Draw $k-1$ branches, one from each other terminal to the reference terminal.




Why $k-1$? KCL on a surface around the element: the k terminal currents sum to zero, so only $k-1$ are free. By KVL, the $k-1$ voltages to the reference fix all the others.

Elements with more than two terminals


A k-terminal element

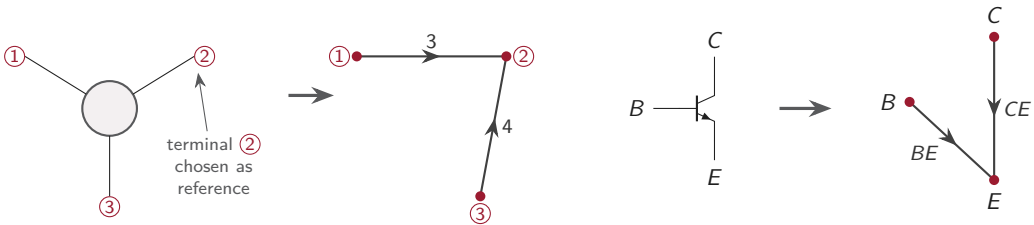Choose one terminal as its reference (arbitrary). Draw $k-1$ branches, one from each other terminal to the reference terminal.



Why $k-1$? KCL on a surface around the element: the k terminal currents sum to zero, so only $k-1$ are free. By KVL, the $k-1$ voltages to the reference fix all the others. A transistor: emitter as reference, two branches.


The general case

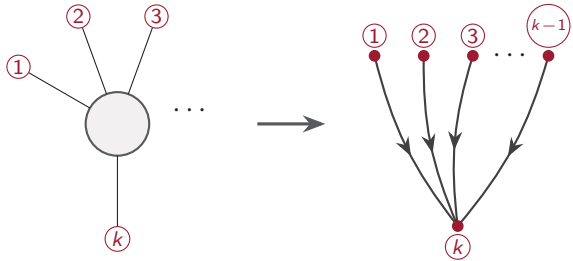

a k-terminal element $k-1$ **branches, all to terminal** k


A dependent source needs nothing new: it is already two branches — the branch that senses the controlling variable, and the source branch.

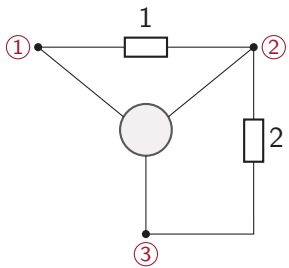Example: a circuit with a 3-terminal element



Elements 1 and 2 have two terminals; the circle has three. Find the graph.

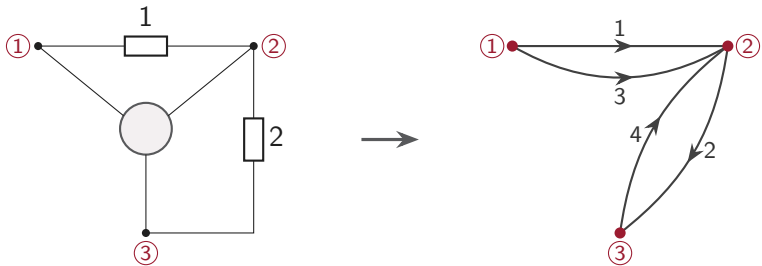
Example: a circuit with a 3-terminal element



Elements 1, 2: one branch each. 3-terminal element, reference terminal at ②: branches 3 (①→②) and 4 (③→②).


$n = 3$, $b = 4$. Two branches may join the same pair of nodes.

KCL on a circuit graph

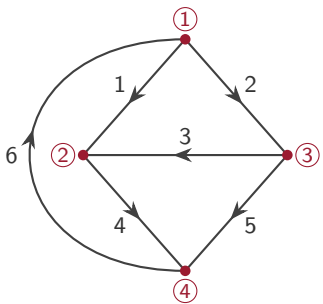

Current along its arrow. At each node:
leaving $+$, entering $-$, sum $= 0$.


KCL on a circuit graph

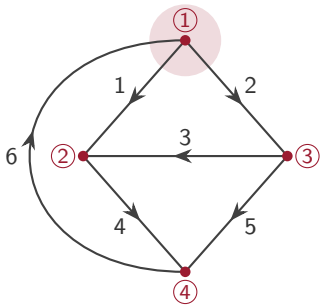

Current along its arrow. At each node:
leaving $+$, entering $-$, sum $= 0$.

$$①: \quad i_1 + i_2 \qquad\qquad - i_6 = 0$$


KCL on a circuit graph

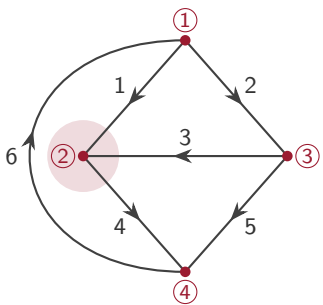

Current along its arrow. At each node:
leaving $+$, entering $-$, sum $= 0$.

$$\begin{aligned} ①: &\quad i_1 + i_2 - i_6 = 0 \\ ②: &\quad -i_1 - i_3 + i_4 = 0 \end{aligned}$$


KCL on a circuit graph

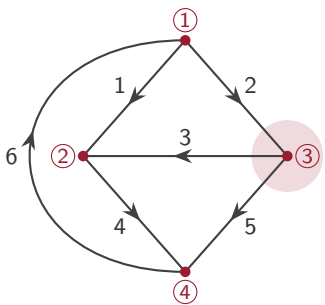

Current along its arrow. At each node:
leaving $+$, entering $-$, sum $= 0$.

$$
\begin{aligned}
① &: \quad i_1 + i_2 - i_6 = 0 \\
② &: \quad -i_1 - i_3 + i_4 = 0 \\
③ &: \quad -i_2 + i_3 + i_5 = 0
\end{aligned}
$$


KCL on a circuit graph

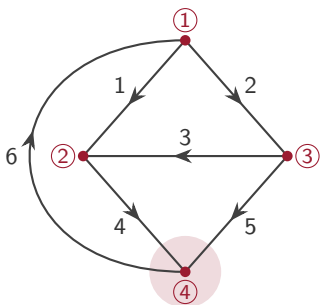

Current along its arrow. At each node:
leaving $+$, entering $-$, sum $= 0$.

$$
\begin{aligned}
&① : \quad i_1 + i_2 - i_6 = 0 \\
&② : \quad -i_1 - i_3 + i_4 = 0 \\
&③ : \quad -i_2 + i_3 + i_5 = 0 \\
&④ : \quad -i_4 - i_5 + i_6 = 0
\end{aligned}
$$

KCL on a circuit graph

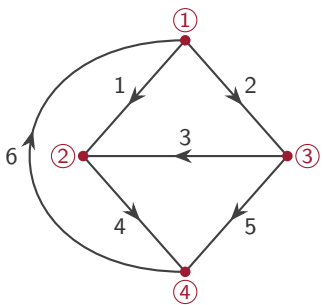

Current along its arrow. At each node:
leaving $+$, entering $-$, sum $= 0$.

$$
\begin{aligned}
① &: \quad i_1 + i_2 - i_6 = 0 \\
② &: \quad -i_1 - i_3 + i_4 = 0 \\
③ &: \quad -i_2 + i_3 + i_5 = 0 \\
④ &: \quad -i_4 - i_5 + i_6 = 0
\end{aligned}
$$

Only the graph was used. Same graph $\Rightarrow$ same KCL equations, whatever the elements are.

From equations to a matrix

Only $+1$, -1 and 0 appear. Rows: nodes. Columns: branches.

$$\begin{array}{c} \\ ① \\ ② \\ ③ \\ ④ \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} \end{array} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \Longleftrightarrow \quad A_a \mathbf{i} = \mathbf{0}$$

A matrix that stores the graph: a circuit matrix. This one is the first and most basic.

From equations to a matrix

Only $+1$, -1 and 0 appear. Rows: nodes. Columns: branches.

$$
\begin{array}{c}
 \\
① \\
② \\
③ \\
④
\end{array}
\begin{array}{c}
\begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\
\begin{bmatrix}
1 & 1 & 0 & 0 & 0 & -1 \\
-1 & 0 & -1 & 1 & 0 & 0 \\
0 & -1 & 1 & 0 & 1 & 0 \\
0 & 0 & 0 & -1 & -1 & 1
\end{bmatrix}
\end{array}
\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}
= \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}
\quad \Longleftrightarrow \quad A_a \mathbf{i} = \mathbf{0}
$$

A row is a node: row ① times $\mathbf{i}$ is KCL at ①.

From equations to a matrix

Only $+1$, -1 and 0 appear. Rows: nodes. Columns: branches.

$$\begin{array}{c} \\ \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \\ \textcircled{4} \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} \end{array} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \Longleftrightarrow \quad A_a \mathbf{i} = \mathbf{0}$$

A column is a branch: one $+1$ (leaves) and one -1 (enters). Column 3: from ③ to ②.

The incidence matrix

Incidence matrix A_a ($n \times b$; j: node, k: branch)

$$a_{jk} = \begin{cases} +1 & \text{if branch } k \text{ leaves node } j, \\ -1 & \text{if branch } k \text{ enters node } j, \\ 0 & \text{otherwise.} \end{cases}$$

With $\mathbf{i} = [\, i_1 \ \cdots \ i_b \,]^T$, the branch current vector: KCL at every node is $A_a\mathbf{i} = \mathbf{0}$.

- The subscript a: *all* nodes have a row.

The incidence matrix

Incidence matrix A_a ($n \times b$; j: node, k: branch)

$$a_{jk} = \begin{cases} +1 & \text{if branch } k \text{ leaves node } j, \\ -1 & \text{if branch } k \text{ enters node } j, \\ 0 & \text{otherwise.} \end{cases}$$

With $\mathbf{i} = [\, i_1 \ \cdots \ i_b \,]^T$, the branch current vector: KCL at every node is $A_a\mathbf{i} = \mathbf{0}$.

- The subscript a: *all* nodes have a row.
- The columns hold the whole graph: from A_a alone you can redraw it, arrows included.

The incidence matrix

Incidence matrix A_a ($n \times b$; j: node, k: branch)

$$a_{jk} = \begin{cases} +1 & \text{if branch } k \text{ leaves node } j, \\ -1 & \text{if branch } k \text{ enters node } j, \\ 0 & \text{otherwise.} \end{cases}$$

With $\mathbf{i} = [\, i_1 \ \cdots \ i_b \,]^T$, the branch current vector: KCL at every node is $A_a\mathbf{i} = \mathbf{0}$.

- The subscript a: *all* nodes have a row.
- The columns hold the whole graph: from A_a alone you can redraw it, arrows included.
- Reversing an arrow flips the sign of that column — nothing else changes.

Review: linear dependence

Linear dependence

$\mathbf{v}_1, \ldots, \mathbf{v}_k$ (same size) are linearly dependent if there are real $\alpha_1, \ldots, \alpha_k$, **not all zero**, with $\alpha_1 \mathbf{v}_1 + \cdots + \alpha_k \mathbf{v}_k = \mathbf{0}$. Otherwise they are linearly independent.

Review: linear dependence

Linear dependence

$\mathbf{v}_1, \ldots, \mathbf{v}_k$ (same size) are linearly dependent if there are real $\alpha_1, \ldots, \alpha_k$, **not all zero**, with $\alpha_1 \mathbf{v}_1 + \cdots + \alpha_k \mathbf{v}_k = \mathbf{0}$. Otherwise they are linearly independent.

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

Dependent or independent?

Review: linear dependence

Linear dependence

$\mathbf{v}_1, \ldots, \mathbf{v}_k$ (same size) are linearly dependent if there are real $\alpha_1, \ldots, \alpha_k$, **not all zero**, with $\alpha_1 \mathbf{v}_1 + \cdots + \alpha_k \mathbf{v}_k = \mathbf{0}$. Otherwise they are linearly independent.

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

independent: $[\alpha_1 \quad -\alpha_2]^T = \mathbf{0}$ only if both are zero.

Review: linear dependence

Linear dependence

$\mathbf{v}_1, \ldots, \mathbf{v}_k$ (same size) are linearly dependent if there are real $\alpha_1, \ldots, \alpha_k$, **not all zero**, with $\alpha_1 \mathbf{v}_1 + \cdots + \alpha_k \mathbf{v}_k = \mathbf{0}$. Otherwise they are linearly independent.

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix}, \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

independent: $[\alpha_1 \quad -\alpha_2]^T = \mathbf{0}$ only if both are zero.

$$\mathbf{v}_1 = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}, \ \mathbf{v}_2 = \begin{bmatrix} 4 \\ 5 \\ 6 \end{bmatrix}, \ \mathbf{v}_3 = \begin{bmatrix} 7 \\ 8 \\ 9 \end{bmatrix}$$

Dependent or independent?

Review: linear dependence

Linear dependence

$\mathbf{v}_1, \ldots, \mathbf{v}_k$ (same size) are linearly dependent if there are real $\alpha_1, \ldots, \alpha_k$, **not all zero**, with $\alpha_1 \mathbf{v}_1 + \cdots + \alpha_k \mathbf{v}_k = \mathbf{0}$. Otherwise they are linearly independent.

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

independent: $[\alpha_1 \quad -\alpha_2]^T = \mathbf{0}$ only if both are zero.

$$\mathbf{v}_1 = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}, \quad \mathbf{v}_2 = \begin{bmatrix} 4 \\ 5 \\ 6 \end{bmatrix}, \quad \mathbf{v}_3 = \begin{bmatrix} 7 \\ 8 \\ 9 \end{bmatrix}$$

dependent: $\mathbf{v}_1 - 2\mathbf{v}_2 + \mathbf{v}_3 = \mathbf{0}$, so $\mathbf{v}_3 = 2\mathbf{v}_2 - \mathbf{v}_1$.

Review: linear dependence

Linear dependence

$\mathbf{v}_1, \ldots, \mathbf{v}_k$ (same size) are linearly dependent if there are real $\alpha_1, \ldots, \alpha_k$, **not all zero**, with $\alpha_1 \mathbf{v}_1 + \cdots + \alpha_k \mathbf{v}_k = \mathbf{0}$. Otherwise they are linearly independent.

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

independent: $\begin{bmatrix} \alpha_1 & -\alpha_2 \end{bmatrix}^T = \mathbf{0}$ only if both are zero.

$$\mathbf{v}_1 = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}, \quad \mathbf{v}_2 = \begin{bmatrix} 4 \\ 5 \\ 6 \end{bmatrix}, \quad \mathbf{v}_3 = \begin{bmatrix} 7 \\ 8 \\ 9 \end{bmatrix}$$

dependent: $\mathbf{v}_1 - 2\mathbf{v}_2 + \mathbf{v}_3 = \mathbf{0}$, so $\mathbf{v}_3 = 2\mathbf{v}_2 - \mathbf{v}_1$.

Rows of M dependent $\Rightarrow$ one equation of $M\mathbf{x} = \mathbf{0}$ follows from the others.
Number of independent rows: the rank. All rows independent: full row rank.

The rows of A_a are always dependent

$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \\ ④ \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} \end{array}$$

The rows of A_a are always dependent

$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \\ ④ \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} \end{array}$$

Each column: one $+1$, one -1.

The rows of A_a are always dependent

$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \\ ④ \\ \hline \text{sum of rows:} \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \left[\begin{array}{cccccc} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{array}\right] \\ \hline \begin{array}{cccccc} 0 & 0 & 0 & 0 & 0 & 0 \end{array} \end{array}$$

Each column: one $+1$, one -1.

$\Rightarrow$ the rows add up to $\mathbf{0}$.

The rows of A_a are always dependent

$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \\ ④ \\ \hline \text{sum of rows:} \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \left[\begin{array}{cccccc} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{array}\right] \\ \hline \begin{array}{cccccc} 0 & 0 & 0 & 0 & 0 & 0 \end{array} \end{array}$$

Each column: one $+1$, one -1.

$\Rightarrow$ the rows add up to $\mathbf{0}$.

One KCL equation is redundant.

The rows of A_a are always dependent

$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \\ ④ \\ \hline \text{sum of rows:} \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \left[\begin{array}{cccccc} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{array}\right] \\ \hline \begin{array}{cccccc} 0 & 0 & 0 & 0 & 0 & 0 \end{array} \end{array}$$

Each column: one $+1$, one -1.

$\Rightarrow$ the rows add up to $\mathbf{0}$.


One KCL equation is redundant.

Reduced incidence matrix A $((n-1) \times b)$

Choose a reference node (ground). Delete its row from A_a.

Example: the reduced incidence matrix of the bridge


Reference node: ④.

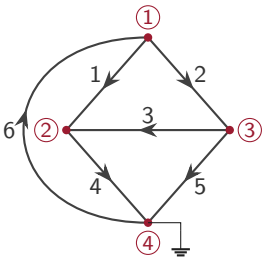

$$A_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$

Example: the reduced incidence matrix of the bridge


Reference node: ④.

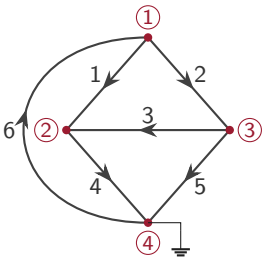

$$A_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$

$$A = \begin{array}{c} \\ ① \\ ② \\ ③ \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} \end{array} \qquad (3 \times 6)$$

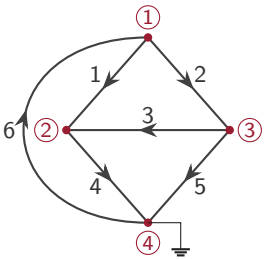Example: the reduced incidence matrix of the bridge



Reference node: ④.


$$A_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$

$$A = \begin{array}{c} \\ ① \\ ② \\ ③ \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} \end{array} \qquad (3 \times 6)$$

Independent rows? Let α_1 row ① + α_2 row ② + α_3 row ③ = $\mathbf{0}$.

Columns 4, 5, 6 have only one nonzero entry each:

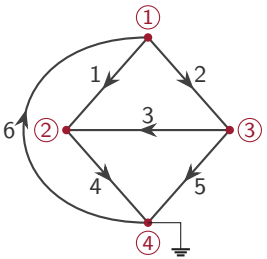Example: the reduced incidence matrix of the bridge



Reference node: ④.

$$A_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$

$$A = \begin{array}{c} \\ ① \\ ② \\ ③ \end{array} \begin{array}{c} \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \\ \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} \end{array} \qquad (3 \times 6)$$

Independent rows? Let α_1 row ① + α_2 row ② + α_3 row ③ = $\mathbf{0}$.

Columns 4, 5, 6 have only one nonzero entry each:

column 4: $\alpha_2 = 0$, column 5: $\alpha_3 = 0$, column 6: $-\alpha_1 = 0$.

All α's are zero: the rows of A are independent.

Deleting the row loses nothing

No equation is lost

The rows add up to $\mathbf{0}$, so row ④ $=-$ (row ① $+$ row ② $+$ row ③)

$$\begin{bmatrix} 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} = - \begin{bmatrix} 0 & 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

Deleting the row loses nothing

No equation is lost

The rows add up to $\mathbf{0}$, so row ④ $= -$ (row ① + row ② + row ③)

$$\begin{bmatrix} 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} = -\begin{bmatrix} 0 & 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

KCL at ④: $-i_4 - i_5 + i_6 = -\left[(i_1 + i_2 - i_6) + (-i_1 - i_3 + i_4) + (-i_2 + i_3 + i_5)\right]$

Deleting the row loses nothing

No equation is lost

The rows add up to $\mathbf{0}$, so row ④ $= -$ (row ① + row ② + row ③)

$$\begin{bmatrix} 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} = -\begin{bmatrix} 0 & 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

KCL at ④: $-i_4 - i_5 + i_6 = -\left[(i_1 + i_2 - i_6) + (-i_1 - i_3 + i_4) + (-i_2 + i_3 + i_5)\right]$

KCL at ①, ②, ③ $\Rightarrow$ KCL at ④.

Deleting the row loses nothing

No equation is lost

The rows add up to $\mathbf{0}$, so row ④ $=-$ (row ① + row ② + row ③)

$$\begin{bmatrix} 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} = -\begin{bmatrix} 0 & 0 & 0 & 1 & 1 & -1 \end{bmatrix}$$

KCL at ④: $-i_4 - i_5 + i_6 = -\left[(i_1 + i_2 - i_6) + (-i_1 - i_3 + i_4) + (-i_2 + i_3 + i_5)\right]$

KCL at ①, ②, ③ $\Rightarrow$ KCL at ④.


No part of the graph is lost

Each column of A_a sums to zero, so the deleted row can be rebuilt from A.
A column of A with a **single nonzero** entry is a branch that touches the reference node.


Connected graphs

Connected graph

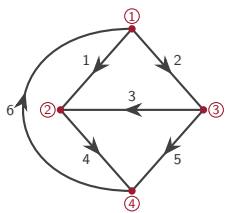Any two nodes are joined by a path of branches, ignoring the arrow directions.
Otherwise the graph falls into separate pieces.



bridge graph: connected

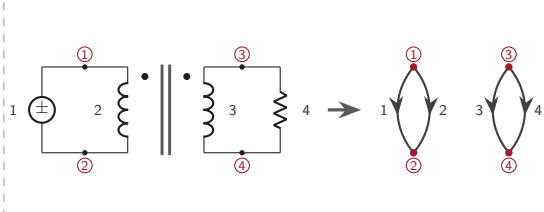


a transformer circuit: two pieces

The windings are coupled only through the core: no branch joins the two sides.

Graphs in separate pieces

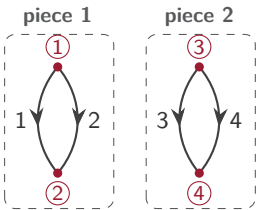Handle each piece on its own, then stack the reduced matrices.




the transformer circuit

	incidence matrix	reference	reduced
piece 1			
piece 2			

Graphs in separate pieces

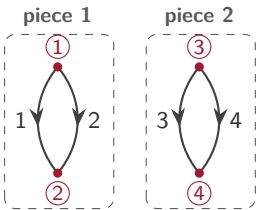Handle each piece on its own, then stack the reduced matrices.



the transformer circuit

incidence matrix **reference** **reduced**

piece 1


$$\begin{array}{c} \\ \textcircled{1} \\ \textcircled{2} \end{array} \begin{array}{c} \begin{array}{cc} 1 & 2 \end{array} \\ \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \end{array}$$

piece 2

$$\begin{array}{c} \\ \textcircled{3} \\ \textcircled{4} \end{array} \begin{array}{c} \begin{array}{cc} 3 & 4 \end{array} \\ \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \end{array}$$

Graphs in separate pieces

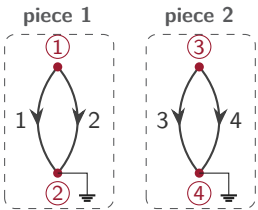Handle each piece on its own, then stack the reduced matrices.




the transformer circuit

	incidence matrix	reference	reduced
piece 1	$\begin{array}{c} \\ ① \\ ② \end{array}\begin{bmatrix} 1 & 2 \\ 1 & 1 \\ \cancel{1} & \cancel{1} \end{bmatrix}$	delete row ②	$A_1 = ① \begin{bmatrix} 1 & 2 \\ 1 & 1 \end{bmatrix}$
piece 2	$\begin{array}{c} \\ ③ \\ ④ \end{array}\begin{bmatrix} 3 & 4 \\ 1 & 1 \\ \cancel{1} & \cancel{1} \end{bmatrix}$	delete row ④	$A_2 = ③ \begin{bmatrix} 3 & 4 \\ 1 & 1 \end{bmatrix}$

Graphs in separate pieces

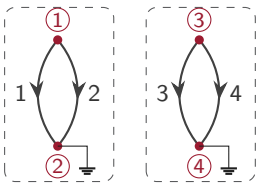Handle each piece on its own, then stack the reduced matrices.



the transformer circuit

incidence matrix **reference** **reduced**

piece 1

$$\begin{matrix} & 1 & 2 \\ ① & 1 & 1 \\ ② & 1 & 1 \end{matrix}$$

delete row ② $A_1 = ①$ $\begin{matrix} & 1 & 2 \\ & 1 & 1 \end{matrix}$

piece 2

$$\begin{matrix} & 3 & 4 \\ ③ & 1 & 1 \\ ④ & 1 & 1 \end{matrix}$$


delete row ④ $A_2 = ③$ $\begin{matrix} & 3 & 4 \\ & 1 & 1 \end{matrix}$

Stack: $A = \begin{bmatrix} A_1 & 0 \\ 0 & A_2 \end{bmatrix} = \begin{matrix} \\ ① \\ ③ \end{matrix} \begin{matrix} \begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \\ \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix} \end{matrix}$

$i_1 + i_2 = 0, \quad i_3 + i_4 = 0$

Graphs in separate pieces

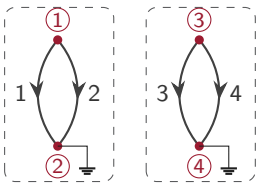Handle each piece on its own, then stack the reduced matrices.



the transformer circuit

incidence matrix **reference** **reduced**

piece 1 $\begin{matrix} \\ ① \\ ② \end{matrix}\begin{bmatrix} 1 & 2 \\ 1 & 1 \\ \cancel{1} & \cancel{1} \end{bmatrix}$ delete row ② $A_1 = \begin{matrix} ① \end{matrix}\begin{bmatrix} 1 & 2 \\ 1 & 1 \end{bmatrix}$

piece 2 $\begin{matrix} \\ ③ \\ ④ \end{matrix}\begin{bmatrix} 3 & 4 \\ 1 & 1 \\ \cancel{1} & \cancel{1} \end{bmatrix}$ delete row ④ $A_2 = \begin{matrix} ③ \end{matrix}\begin{bmatrix} 3 & 4 \\ 1 & 1 \end{bmatrix}$

Stack: $A = \begin{bmatrix} A_1 & 0 \\ 0 & A_2 \end{bmatrix} = \begin{matrix} ① \\ ③ \end{matrix}\begin{bmatrix} 1 & 2 & 3 & 4 \\ 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix}$ $\quad i_1 + i_2 = 0, \quad i_3 + i_4 = 0$

p pieces: p reference nodes, so A has $n - p$ independent rows. Here $4 - 2 = 2$.

KCL of a circuit graph


$$A\mathbf{i} = \mathbf{0}$$

$A \in \mathbb{R}^{(n-1)\times b}$	reduced incidence matrix
$\mathbf{i} \in \mathbb{R}^{b}$	branch current vector

For a connected graph: $n-1$ independent KCL equations,
and every other KCL equation of the circuit follows from them.


Separate pieces: one reference node per piece, $n-p$ rows.

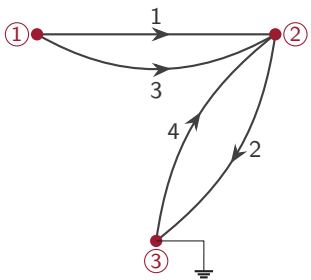Example: KCL for the circuit with a 3-terminal element



Reference node: ③.

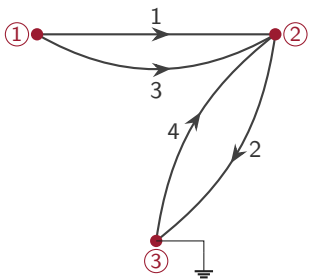
Example: KCL for the circuit with a 3-terminal element



$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \end{array} \begin{array}{c} \begin{array}{cccc} 1 & 2 & 3 & 4 \end{array} \\ \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 1 & -1 & -1 \\ 0 & -1 & 0 & 1 \end{bmatrix} \end{array}$$

Reference node: ③.

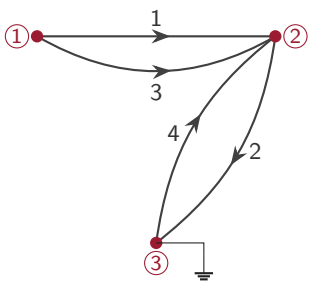Example: KCL for the circuit with a 3-terminal element




Reference node: ③.

$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \end{array} \begin{array}{c} \begin{array}{cccc} 1 & 2 & 3 & 4 \end{array} \\ \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 1 & -1 & -1 \\ 0 & -1 & 0 & 1 \end{bmatrix} \end{array}$$

$$A = \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 1 & -1 & -1 \end{bmatrix}$$

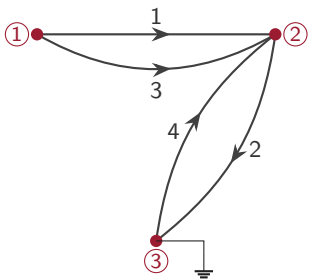Example: KCL for the circuit with a 3-terminal element



Reference node: ③.


$$A_a = \begin{array}{c} \\ ① \\ ② \\ ③ \end{array} \begin{array}{c} \begin{array}{cccc} 1 & 2 & 3 & 4 \end{array} \\ \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 1 & -1 & -1 \\ 0 & -1 & 0 & 1 \end{bmatrix} \end{array}$$

$$A = \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 1 & -1 & -1 \end{bmatrix}$$

$$i_1 + i_3 = 0, \qquad -i_1 + i_2 - i_3 - i_4 = 0$$

Columns 1 and 3 are equal: same nodes, same direction. Reference terminal (②) and reference node (③): two separate choices.

Branch voltages and node voltages

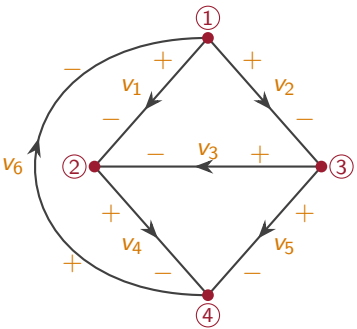


Branch voltage v_k



$+$ at the tail: i_k enters at $+$. $b = 6$

Branch voltages and node voltages

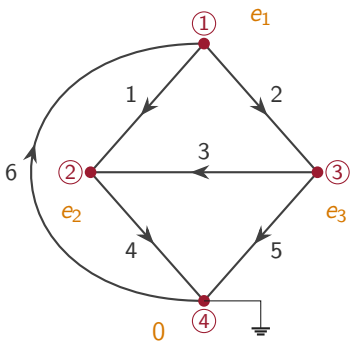

Branch voltage v_k




$+$ at the tail: i_k enters at $+$. $b = 6$

Node voltage e_k


Node k with respect to the reference.
Reference: $e = 0$. $n - 1 = 3$

Each e_k: $+$ at node k, $-$ at the reference ④.

KVL on a circuit graph

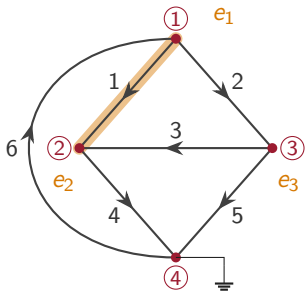


Loop ① → ② → ④ → ①:

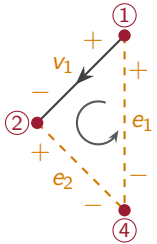


$$v_1 + e_2 - e_1 = 0$$

$$\Rightarrow v_1 = e_1 - e_2$$

KVL on a circuit graph

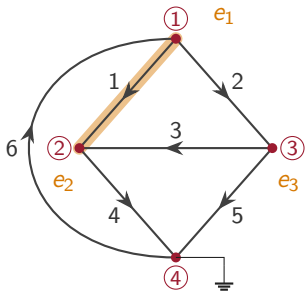

Loop ① → ② → ④ → ①:

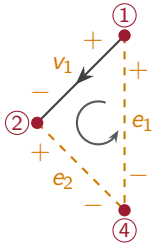


$$v_1 + e_2 - e_1 = 0$$

$$\Rightarrow v_1 = e_1 - e_2$$

Any branch k: tail p, head q

$v_k = e_p - e_q$ — tail minus head ($e = 0$ at the reference)


KVL for all branches

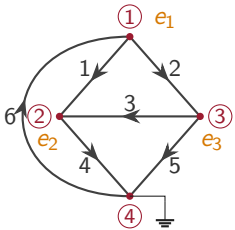

Tail minus head:

$$v_1 = e_1 - e_2 \quad v_4 = e_2$$
$$v_2 = e_1 - e_3 \quad v_5 = e_3$$
$$v_3 = e_3 - e_2 \quad v_6 = -e_1$$

KVL for all branches

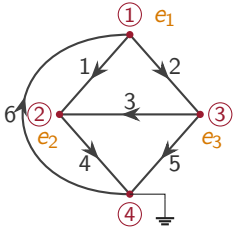


Tail minus head:

$$v_1 = e_1 - e_2 \quad v_4 = e_2$$
$$v_2 = e_1 - e_3 \quad v_5 = e_3$$
$$v_3 = e_3 - e_2 \quad v_6 = -e_1$$

In matrix form:

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix}}_{A^T} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}$$

KVL for all branches

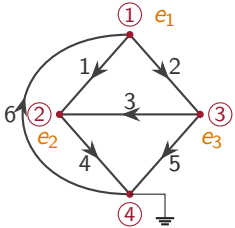

Tail minus head:

$$v_1 = e_1 - e_2 \quad v_4 = e_2$$
$$v_2 = e_1 - e_3 \quad v_5 = e_3$$
$$v_3 = e_3 - e_2 \quad v_6 = -e_1$$

In matrix form:

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix}}_{A^T} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}$$

A^T is the transpose of the reduced incidence matrix A: row k of A^T = column k of A.

KVL in matrix form

$$\mathbf{v} = A^T \mathbf{e}$$

$\mathbf{v} \in \mathbb{R}^b$ branch voltage vector

$\mathbf{e} \in \mathbb{R}^{n-1}$ node voltage vector

The same A gives KCL ($A\mathbf{i} = \mathbf{0}$) and KVL.

KVL in matrix form

$$\mathbf{v} = A^T \mathbf{e}$$

$\mathbf{v} \in \mathbb{R}^b$ branch voltage vector

$\mathbf{e} \in \mathbb{R}^{n-1}$ node voltage vector

The same A gives KCL ($A\mathbf{i} = \mathbf{0}$) and KVL.

- Know the $n-1$ node voltages $\Rightarrow$ know all b branch voltages.

KVL in matrix form

$$\mathbf{v} = A^T \mathbf{e}$$

$\mathbf{v} \in \mathbb{R}^b$ branch voltage vector

$\mathbf{e} \in \mathbb{R}^{n-1}$ node voltage vector

The same A gives KCL ($A\mathbf{i} = \mathbf{0}$) and KVL.

- Know the $n-1$ node voltages $\Rightarrow$ know all b branch voltages.
- KVL puts no constraint on $\mathbf{e}$: any $\mathbf{e}$ satisfies KVL around every loop. Loop 1, 3, 2: $v_1 - v_3 - v_2 = (e_1 - e_2) - (e_3 - e_2) - (e_1 - e_3) = 0$

KVL in matrix form

$$\mathbf{v} = A^T \mathbf{e}$$


$\mathbf{v} \in \mathbb{R}^b$ branch voltage vector

$\mathbf{e} \in \mathbb{R}^{n-1}$ node voltage vector


The same A gives KCL ($A\mathbf{i} = \mathbf{0}$) and KVL.

- Know the $n-1$ node voltages $\Rightarrow$ know all b branch voltages.
- KVL puts no constraint on $\mathbf{e}$: any $\mathbf{e}$ satisfies KVL around every loop. Loop 1, 3, 2: $v_1 - v_3 - v_2 = (e_1 - e_2) - (e_3 - e_2) - (e_1 - e_3) = 0$
- So node voltages are good unknowns: only $n-1$, free, KVL automatic — the idea behind node analysis.

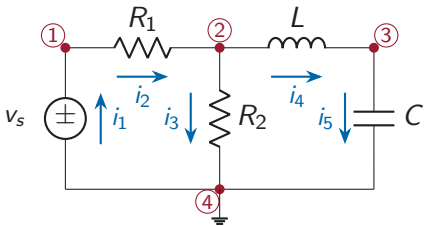
Example: branch voltages from node voltages



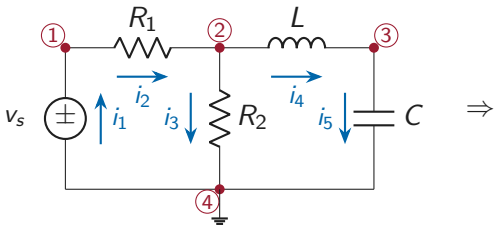
Example: branch voltages from node voltages




$\Rightarrow$

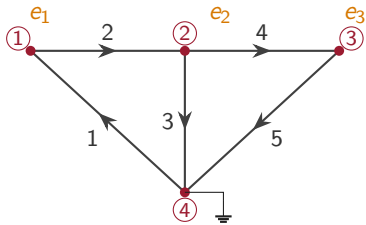

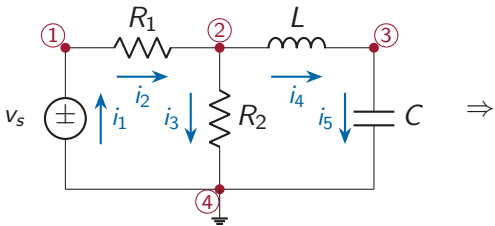Example: branch voltages from node voltages




$\Rightarrow$

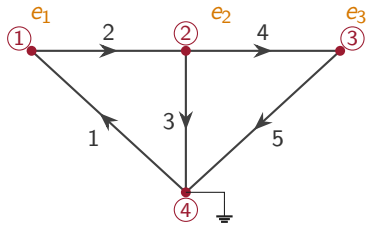


$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix}$$

reference ④

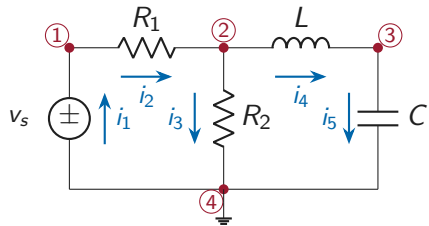Example: branch voltages from node voltages



$\Rightarrow$

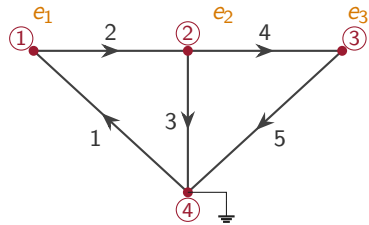

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix}$$

reference ④

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -e_1 \\ e_1 - e_2 \\ e_2 \\ e_2 - e_3 \\ e_3 \end{bmatrix}$$

Tellegen's theorem

Tellegen's theorem

In any circuit, with associated references,

$$\mathbf{i}^T \mathbf{v} = \sum_{k=1}^{b} v_k \, i_k = 0 \qquad \text{at every instant } t.$$

Tellegen's theorem

Tellegen's theorem


In any circuit, with associated references,

$$\mathbf{i}^T\mathbf{v} = \sum_{k=1}^{b} v_k\, i_k = 0 \qquad \text{at every instant } t.$$

$v_k i_k$ = power absorbed by branch k. Total absorbed power = 0:
conservation of power — what some branches deliver, the others absorb.

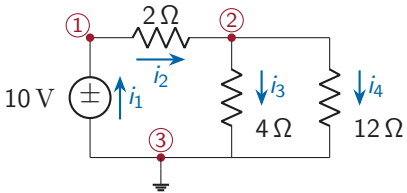Example: checking Tellegen's theorem


Find v_k and i_k of every branch with node voltages, then check $\sum_k v_k i_k = 0$.



reference ③; + of v_k at the tail of each arrow

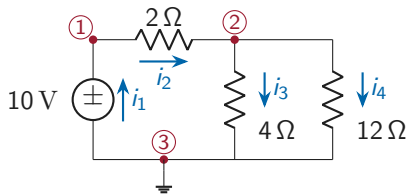Example: checking Tellegen's theorem

Find v_k and i_k of every branch with node voltages, then check $\sum_k v_k i_k = 0$.




Node voltages: $e_1 = 10\,\mathrm{V}$ (source), e_2 unknown.

reference ③; + of v_k at the tail of each arrow

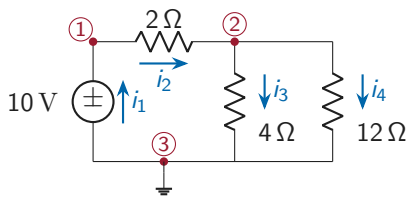Example: checking Tellegen's theorem

Find v_k and i_k of every branch with node voltages, then check $\sum_k v_k i_k = 0$.




reference ③; + of v_k at the tail of each arrow

Node voltages: $e_1 = 10\,\mathrm{V}$ (source), e_2 unknown.

KCL at ②: $-\dfrac{e_1 - e_2}{2} + \dfrac{e_2}{4} + \dfrac{e_2}{12} = 0 \;\Rightarrow\; e_2 = 6\,\mathrm{V}$

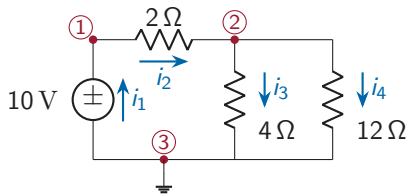Example: checking Tellegen's theorem

Find v_k and i_k of every branch with node voltages, then check $\sum_k v_k i_k = 0$.



reference ③; + of v_k at the tail of each arrow

Node voltages: $e_1 = 10\,\mathrm{V}$ (source), e_2 unknown.


KCL at ②: $-\dfrac{e_1 - e_2}{2} + \dfrac{e_2}{4} + \dfrac{e_2}{12} = 0 \;\Rightarrow\; e_2 = 6\,\mathrm{V}$

$\mathbf{v} = A^T\mathbf{e}$**:** $v_1 = -e_1 = -10$, $v_2 = 4$, $v_3 = v_4 = 6\,\mathrm{V}$

Ohm, KCL at ①: $i_1 = i_2 = 2$, $i_3 = 1.5$, $i_4 = 0.5\,\mathrm{A}$

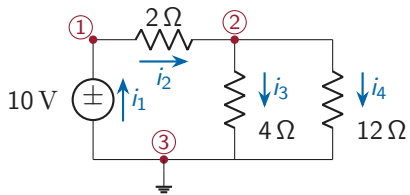Example: checking Tellegen's theorem

Find v_k and i_k of every branch with node voltages, then check $\sum_k v_k i_k = 0$.



Node voltages: $e_1 = 10\,\mathrm{V}$ (source), e_2 unknown.

KCL at ②: $-\dfrac{e_1 - e_2}{2} + \dfrac{e_2}{4} + \dfrac{e_2}{12} = 0 \;\Rightarrow\; e_2 = 6\,\mathrm{V}$

v $= A^T$**e:** $v_1 = -e_1 = -10$, $v_2 = 4$, $v_3 = v_4 = 6\,\mathrm{V}$

Ohm, KCL at ①: $i_1 = i_2 = 2$, $i_3 = 1.5$, $i_4 = 0.5\,\mathrm{A}$

reference ③; + of v_k at the tail of each arrow

branch	element	v_k (V)	i_k (A)	$v_k i_k$ (W)
1	source	−10	2	−20
2	2 Ω	4	2	8
3	4 Ω	6	1.5	9
4	12 Ω	6	0.5	3
			sum	0

$v_1 < 0$: its + (tail) is at ③.
The source delivers 20 W; the resistors absorb $8 + 9 + 3 = 20\,\mathrm{W}$.


Looking ahead: why node voltages?

$2b$ unknowns (all v_k, i_k), $2b$ equations: b element, $n-1$ KCL, $b-n+1$ KVL.

e
$n-1$
unknowns


Looking ahead: why node voltages?

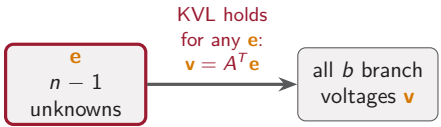$2b$ unknowns (all v_k, i_k), $2b$ equations: b element, $n-1$ KCL, $b-n+1$ KVL.




Looking ahead: why node voltages?

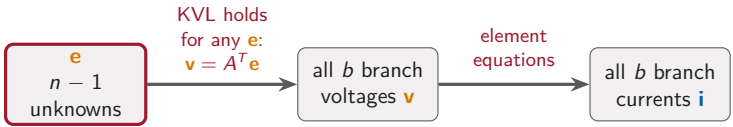$2b$ unknowns (all v_k, i_k), $2b$ equations: b element, $n-1$ KCL, $b-n+1$ KVL.




Looking ahead: why node voltages?

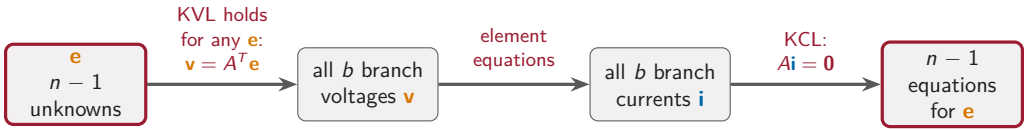$2b$ unknowns (all v_k, i_k), $2b$ equations: b element, $n-1$ KCL, $b-n+1$ KVL.



Looking ahead: why node voltages?

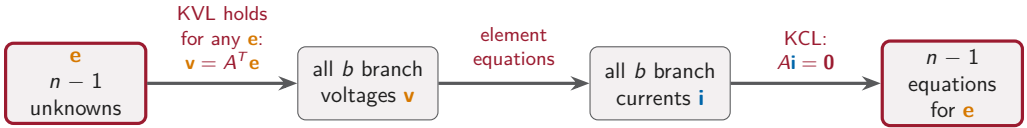$2b$ unknowns (all v_k, i_k), $2b$ equations: b element, $n-1$ KCL, $b-n+1$ KVL.



$2b$ unknowns $\rightarrow$ $n-1 < b$: n nodes take $n-1$ branches to join; each loop adds one.

Solve for **e**; everything else follows. Node analysis — coming soon.

Summary

- $2b$ equations: b **element** equations and b **interconnection** equations (KCL, KVL). The second group depends only on the graph.
- The graph: number the branches, give each an arbitrary arrow, number the nodes. A k-terminal element becomes $k-1$ branches.
- **Incidence matrix** A_a ($n \times b$): $+1$ leaves, -1 enters. KCL: $A_a\mathbf{i} = \mathbf{0}$. Its rows always sum to zero.
- **Reduced incidence matrix** A: delete the reference node's row. For a connected graph, $A\mathbf{i} = \mathbf{0}$ gives exactly the $n-1$ independent KCL equations.
- **KVL**: $\mathbf{v} = A^T\mathbf{e}$ — tail minus head. No constraint on the node voltages $\mathbf{e}$.
- **Tellegen**: in any circuit $\mathbf{i}^T\mathbf{v} = \sum v_k i_k = 0$ — conservation of power.
- **Why**: with $\mathbf{e}$ as unknowns KVL holds automatically; $n-1$ unknowns are enough — the idea of node analysis.

Next lecture

Planar graphs and meshes

The mesh matrix M: KVL as $M\mathbf{v} = \mathbf{0}$, and mesh currents with $\mathbf{i} = M^T \mathbf{i}_M$ — the counterpart of $\mathbf{v} = A^T \mathbf{e}$.

Questions?